

<b>Title of the Exercise:</b> Parallel RLC Circuit
<b>Date:</b> 4.9.2020
<b>Aim:</b> To Simulate the dynamic model of a RLC circuit and plots Voltage and current at various terminals and also analyze theoretical results.
<b>Tool used:</b> MATLAB
<div data-bbox="386 468 812 665"> </div> <div data-bbox="909 420 1323 672"> </div> <p data-bbox="233 655 373 724"><b>Electrical Circuit:</b></p> <p data-bbox="233 730 641 766"><b>Parameters used for the study:</b></p> <p data-bbox="233 766 950 802">Input: <math>R_s = 50\text{ohm}</math>, <math>L = 0.1\text{H}</math>, <math>C = 1000\text{e-6F}</math>, <math>V=100\text{ Volts}</math></p>
<b>Theoretical Analysis:</b> It's a transient circuit with a current source. We use transient circuit analysis to determine the values of current and volaage for the capacitor and inductor.
<b>Calculations (Predetermination):</b>

## Theoretical Analysis

Given:  $R = 50 \Omega$ ,  $L = 0.1 \text{ H}$ ,  $C = 1000 \times 10^{-6} \text{ F}$

$$V = 100 \text{ V}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.1 \times \left(\frac{1}{1000}\right)}} = 1000$$

$$\alpha = \frac{1}{2RC} = \frac{1 \times 1000}{2 \times 50} = 10$$

$$\omega_0 > \alpha, \rightarrow \omega = \sqrt{1000^2 - 10^2} = 99.5$$

$V_C$  can be expressed as

$$V_C = e^{-\alpha t} (B_1 \cos \omega t + B_2 \sin \omega t)$$

$$V_C(0) = 0 = B_1$$

$$\rightarrow B_1 = 0 //$$

differentiating  $V_C$  w.r.t  $t$

$$\begin{aligned} \frac{dV_C}{dt} = & -10 e^{-10t} (B_1 \cos 99.5t + B_2 \sin 99.5t) \\ & + 99.5 \times e^{-10t} (-B_1 \sin 99.5t + B_2 \cos 99.5t) \end{aligned}$$

$$\text{at } t=0 \quad \left. \frac{dV_C}{dt} \right|_{t=0} = \frac{i_C}{C} = 2000 \quad \left| i_C = C \frac{dV_C}{dt} \right.$$

$$\left. \frac{dV_C}{dt} \right|_{t=0} = -10 B_1 + 99.5 (-B_1 + B_2) \quad | B_1 = 0$$

$$B_2 = 20.10$$

$$V_c = (20.1 \sin 99.5t) e^{-10t}$$

$$V_L = (20.1 \sin 99.5t) e^{-10t}$$

Solving for other values, we will get

$$i_s(t) = 2 - 0.401 e^{-10t} \sin 99.5t$$

$$i_L(t) = 2t e^{-10t} (-2 \cos 99.5t - 0.201 \sin 99.5t)$$

$$i_C(t) = e^{-10t} (2 \cos 99.5t - 0.201 \sin 99.5t)$$

**Procedure for simulation study:**

Step 1-Initialize the input parameters and write coding for the as per requirement of plots in m file and save it.

Step 2-open new Simulink and make mathematical modelling as per circuit diagram and save it.

Step 3-Run the m file first ,after that run Simulink file.


Step 4 -View the result in Scope.

Step 5- Again run m file and view the plots.

Step 6-Make various plots and write the Results.

**Simulation Diagram and m.file coding :**

**Simulation rendered wave form:-**

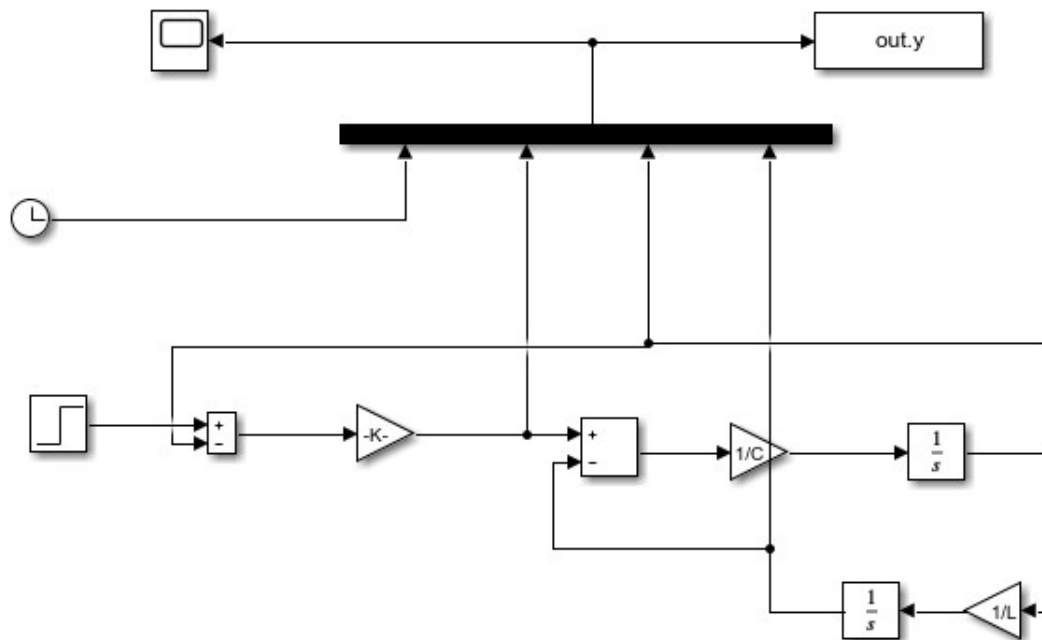


**M.file coding:**

```
Rs = 50;
L= 0.1;
C= 1000e-6;
vS= 100;
tdealy= 0.05;
vCo= 0;
iLo= 0;
tstop=0.5;
disp('run simulation')
keyboard
%plot(figsize(10,6))
subplot(3,1,1)
nexttile
plot(out.y.signals.values(:,1),out.y.signals.values(:,2),'b--o')
title('source current')
ylabel('is in Amp')
nexttile
plot(out.y.signals.values(:,1),out.y.signals.values(:,3),'g.')
title('capacitor voltage')
ylabel('vC in volts')
nexttile
plot(out.y.signals.values(:,1),out.y.signals.values(:,4),'y--o')
title('inductor current')
ylabel('iL in Amp')
xlabel('time in secs')
%set(gcf,'position',[0,0.1,400,600])
```
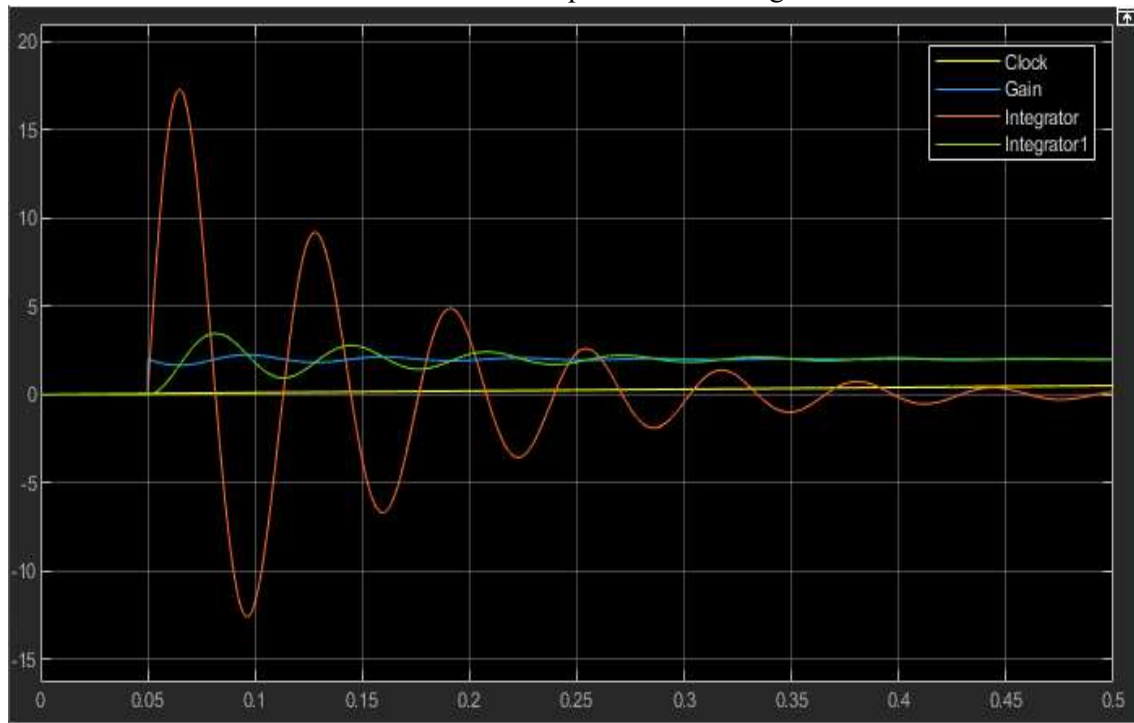
### Results and Discussions:

This section contains both waveforms with respect to time along with the theoretical value.



Simulation rendered waveforms

### Comparison (Observations):

Time	Theoretical Value(Ic)	Simulation(Ic)	Theoretical Value(Vc)	Simulation(Vc)
0	2	2	0	0
0.5	0.007673	0.007673	0.10337	0.10337
0.25	0.142	0.14199	0.6940	0.6940
0.025	1.5493	1.5493	0.6794	0.6794

**Conclusion:** The theoretical value is the same as the simulation results.

**Inference:** The analysis of the parallel RLC circuit dynamic model provides the following inferences:

- As the time increases, after a certain amount of time the value of capacitor voltage and inductor current doesn't change
- The value of  $\omega$  is less than the value of  $\alpha$  therefore it is a critically underdamped circuit.

**Reference:**NIL